

Worksheet for Subject- Science

Class-X

Topic – Ohm's Law

Q1 explain the ohms law with circuit diagram

Q2 if 3 amp current flow in a wire and resistance of wire 4 ohm then calculate the potential difference

Q3 Define 1 amp .

Q4 if 10 electron are flow in 2 sec then calculate the current