

Q1 A coil which has a resistance of 4.2 ohm is immersed into water if 2 amp current is flowing through it for 10 minutes then how much heat will produced ?

Q2 When we switch on the lights of house one by one then what will be the it's effect on the resistance of the circuit and current ?